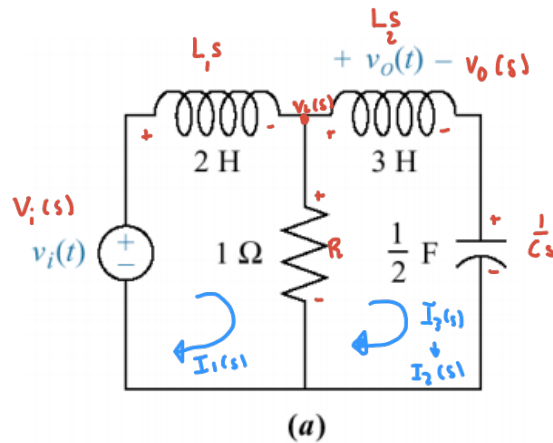


SFWRENG3DX4 Tutorial Quiz 2 Wednesday: Electrical Transfer Functions

1. System Models: Circuits



Consider the circuit show above.

- (5 marks) Write down the loop (mesh) equations that you would use to solve to get the transfer function from the input $v_i(t)$ to the output $v_o(t)$.
- (5 marks) Solve for the transfer function $G(s) = \frac{V_o(s)}{V_i(s)}$.

$$a) \quad V_i(s) - L_1 s I_1(s) - R[I_1(s) - I_2(s)] = 0$$

$$V_i(s) = L_1 s I_1(s) + R[I_1(s) - I_2(s)] \rightarrow V_i(s) = 2s I_1(s) + I_1(s) - I_2(s)$$

$$-L_2 s I_2(s) - \frac{1}{Cs} I_2(s) + R[I_2(s) - I_1(s)] = 0$$

$$0 = L_2 s I_2(s) + \frac{1}{Cs} I_2(s) - R[I_2(s) - I_1(s)] \rightarrow 0 = 3s I_2(s) + \frac{2}{s} I_2(s) + I_1(s) - I_2(s)$$

$$b) \quad \begin{bmatrix} 2s+1 & -1 \\ 1 & 3s+\frac{2}{s}-1 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} V_i(s) \\ 0 \end{bmatrix}$$

$$I_2(s) = \frac{\det A_2}{\det A} = \det \begin{bmatrix} 2s+1 & V_i(s) \\ 1 & 0 \end{bmatrix} \div \det \begin{bmatrix} 2s+1 & -1 \\ 1 & 3s+\frac{2}{s}-1 \end{bmatrix} \rightarrow I_2(s) = \frac{-V_i(s)}{(2s+1)(3s+\frac{2}{s}-1) + 1}$$

$$V_o(s) = 3s I_2(s) \rightarrow V_o(s) = \frac{-3s V_i(s)}{6s^2 + s + \frac{2}{s} + 3}$$

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{-3s}{6s^2 + s + \frac{2}{s} + 3} \rightarrow G(s) = \frac{-\frac{1}{2}s}{s^2 + \frac{1}{6}s + \frac{1}{3s} + \frac{1}{2}}$$